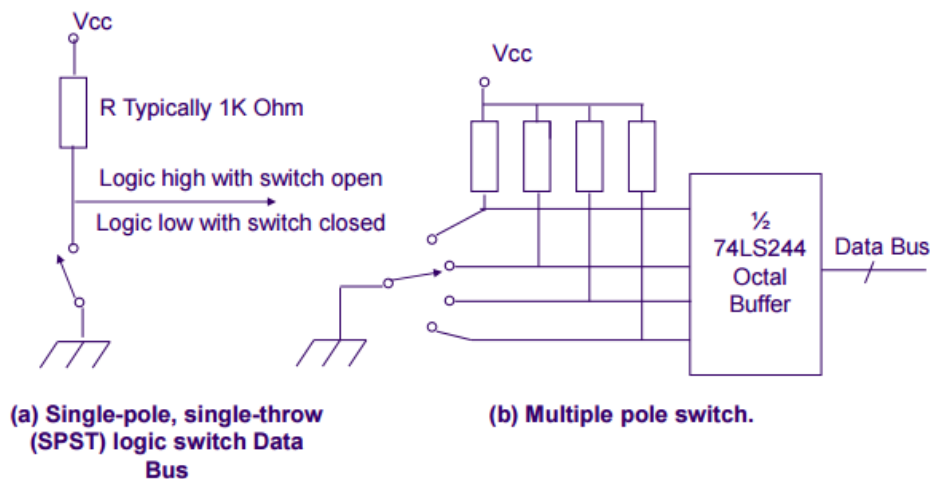


6. I/O Devices


COMP2121 • KC Notes

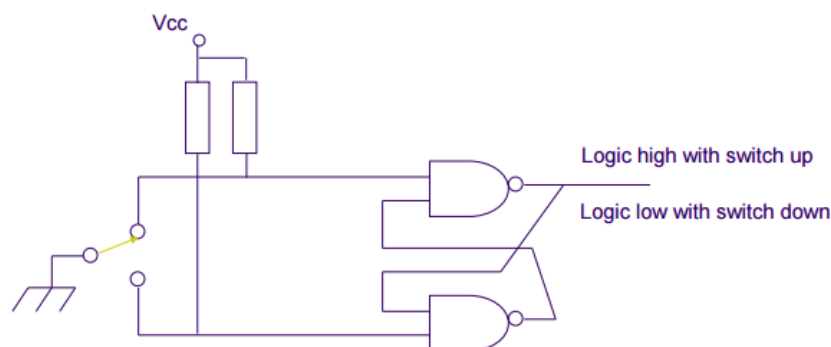6.1 Input Switches

- **Input Switches:** Most basic binary input devices – **high or low** depending on switch position
- **Pull-up resistors** are needed in each switch to **provide high logic level when switch is open**





- **Switch bounce:** a **transient behaviour** causing erroneous counting in software
 - Switches bounce for 5-10ms, needs **debouncing**
- **Software debouncing:**
 - **“Wait and See”:** software waits for 20 to 100ms and tests if the switch is still low
 - **Counter-based:** Initialise a counter to 10, and at the detection of a logic low, poll the switch every 1ms and decrement if a low is polled, increment if a high is polled.
 - 0 = switch closed for at least 10ms
 - 20 = switch has been open for at least 10ms
- NAND Latch Debouncer



6.2 Arrays of Switches and the Keypad

- **Linear/1D Array of Switches:** software scans through the array and outputs a **3-bit sequence (S2,S1,S0)** from 000 to 111 **to select a switch**.
 - The selected switch input is scanned one bit at a time by the multiplexer
- **Matrix/2D Array of Switches:** (A2,A1,A0) selects a switch's A position, (S2,S1,S0) selects a switch's B position
 - i.e. **output (A2,A1,A0)** and then **scan (S2,S1,S0)**, repeat for all A's
 - Switches are connected **at each intersection of vertical/horizontal line**
 - Closing the switch **connects** the two lines

One-Dimensional Array of Switches

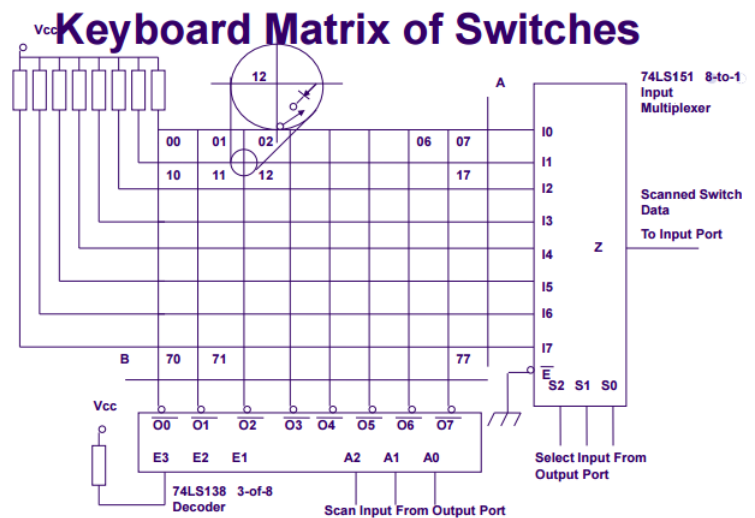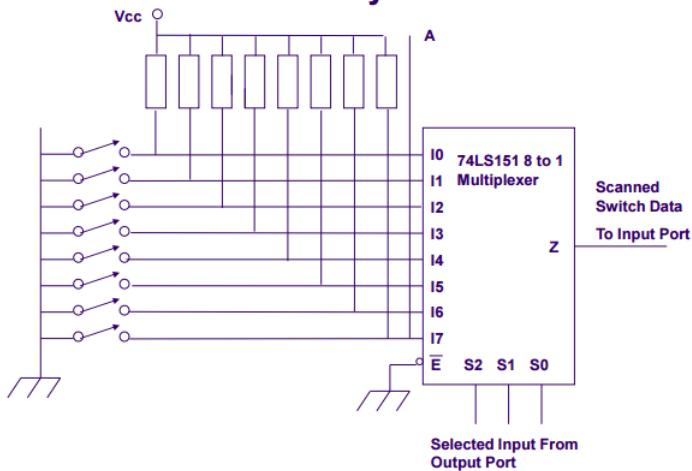

- Diode prevents **ghosting**, when several keys are pushed at once
 - Diodes in the switches eliminate ghosting by preventing current flow down a row

6.3 Dot Matrix LCD

- A **controller** is used for **communication between LCD and MPU**. It has its own internal character generator ROM, and display functions are controllable **using instructions**
- Connected to 14 pins:
 - **DB4-7:** high order data bus used bi-directionally, DB7 used as a busy flag
 - **DB0-3:** low order data bus
 - **E:** Enable bit, operation start signal for data read and write
 - **R/W:** Signal to select read (1) or write (0)
 - **RS:** Register select (write instruction register or write/read data register)
 - **Vee:** terminal for LCD drive power source, **Vcc:** +5V, **Vss:** 0V
- **Instruction register:** instruction codes like Cursor shift, as well as addresses in the Display Data RAM (DD RAM) or character generator RAM (CG RAM)
- **Data register:** Temporarily store data to be read/written to/from DD RAM
- LCD module may be busy (busy flag) with an internal operation. Also needs to be **initialised** in software before use.